



NAME \_\_\_\_\_

# LABEL IT

Using terms from the word bank, label the components of the electrical circuit.

NEGATIVE TERMINAL	POSITIVE TERMINAL	POWER SOURCE
LOAD	RUBBER INSULATION	COPPER WIRE